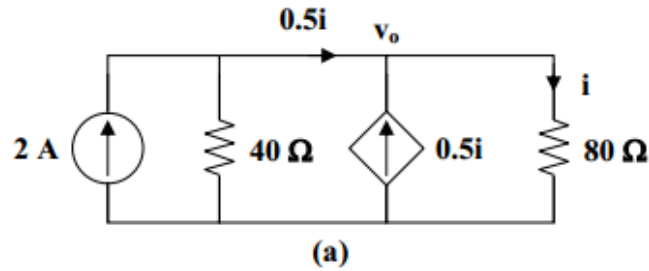


جواب تمرینات سری چهارم

-۲

Before $t = 0$, the circuit has reached steady state so that the capacitor acts like an open circuit. The circuit is equivalent to that shown in Fig. (a) after transforming the voltage source.




$$0.5i = 2 - \frac{v_o}{40}, \quad i = \frac{v_o}{80}$$

$$\text{Hence, } \frac{1}{2} \frac{v_o}{80} = 2 - \frac{v_o}{40} \longrightarrow v_o = \frac{320}{5} = 64$$


$$i = \frac{v_o}{80} = \underline{\underline{0.8 \text{ A}}}$$

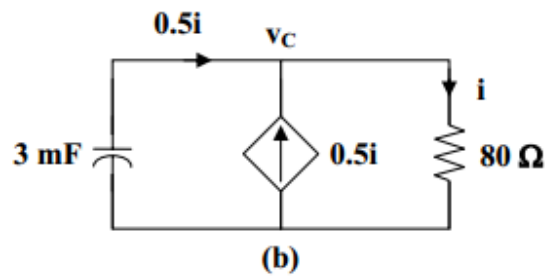After $t = 0$, the circuit is as shown in Fig. (b).



$$v_C(t) = v_C(0)e^{-t/\tau}, \quad \tau = R_{th}C$$

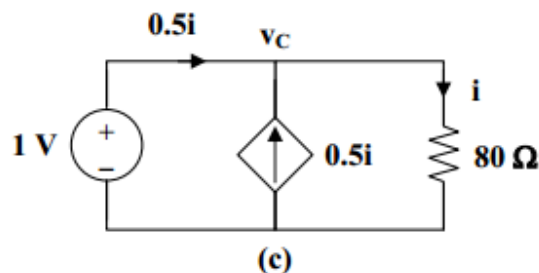To find R_{th} , we replace the capacitor with a 1-V voltage source as shown in Fig. (c).



$$i = \frac{v_c}{80} = \frac{1}{80}, \quad i_o = 0.5i = \frac{0.5}{80}$$


$$R_{th} = \frac{1}{i_o} = \frac{80}{0.5} = 160 \, \Omega, \quad \tau = R_{th}C = 480$$

$$v_c(0) = 64 \, V$$

$$v_c(t) = 64 e^{-t/480}$$

$$0.5i = -i_c = -C \frac{dv_c}{dt} = -3 \left(\frac{1}{480} \right) 64 e^{-t/480}$$
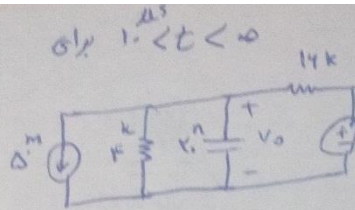
$$i(t) = \underline{0.8 e^{-t/480} \, u(t) A}$$




چون ولتاژ خازن تغییراتی ندارد پس ولتاژ خازن در $V_o(1.0^-)$ برابر است با ولتاژ خازن در $V_o(1.0^+)$ پس داریم:

از مدار V_o برای $0 < t < 1.0\mu$ به دست می آید (توسط)


$$V_o(1.0^-) = -2.0(1 - e^{-12500 \times 1.0}) = -1.248$$

$V_o(\infty) = ?$

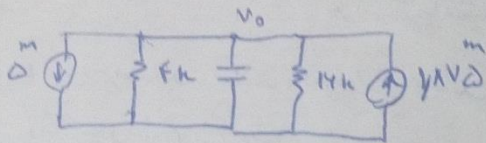

$$R_{eq} = 14 \parallel 2 = 2.12^k$$

$$I_{eq} = 2 - 11.8V/2 = 2.12^m$$

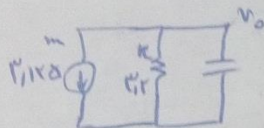


$$V_o(\infty) = 2.12^k \times 14^m = -1.0$$

$$\tau = R_{eq} C = 2.12^k \times 2.0^n = 42^{\mu}$$

$$V_o(t) = -1.0 + (-1.248 + 1.0) e^{-\frac{(t-1.0\mu)}{42^{\mu}}}$$
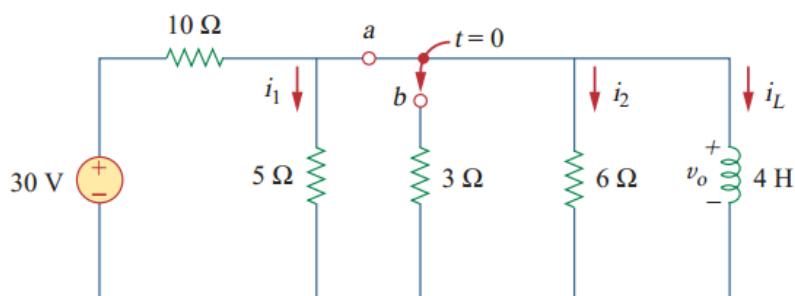
$$V_o(t) = \begin{cases} 0 & t < 0 \\ -2.0(1 - e^{-12500t}) & 0 < t < 1.0\mu \\ -1.0 + 9.1752e^{-12542(t-1.0\mu)} & 1.0\mu < t < \infty \end{cases}$$



- (a) When the switch is in position A, the 5-ohm and 6-ohm resistors are short-circuited so that

$$\underline{i_1(0) = i_2(0) = v_o(0) = 0}$$

but the current through the 4-H inductor is $i_L(0) = 30/10 = 3\text{ A}$.

- (b) When the switch is in position B,

$$R_{Th} = 3 // 6 = 2\Omega, \quad \tau = \frac{L}{R_{Th}} = 4/2 = 2\text{ sec}$$


$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau} = 0 + 3e^{-t/2} = \underline{3e^{-t/2}\text{ A}}$$

$$(c) \quad i_1(\infty) = \frac{30}{10+5} = \underline{2\text{ A}}, \quad i_2(\infty) = -\frac{3}{9}i_L(\infty) = \underline{0\text{ A}}$$

$$v_o(t) = L \frac{di_L}{dt} \longrightarrow \underline{v_o(\infty) = 0\text{ V}}$$


Note that for $t > 0$, $v_o = (10/15)v_c$, where v_c is the voltage across the 25 nF capacitor. Thus we will find v_c first.

$t < 0$

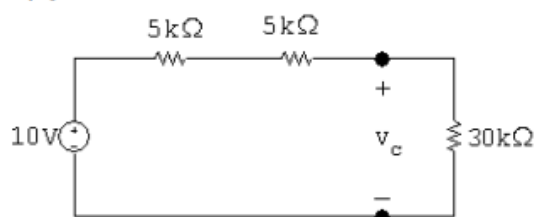

$$v_c(0) = \frac{30}{40}(10) = 7.5 \text{ V}$$

$0 \leq t \leq 0.2 \text{ ms}$:

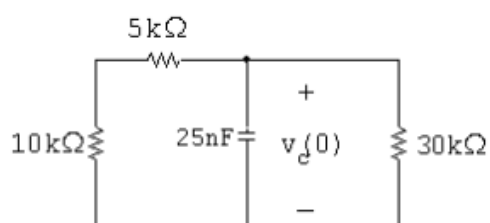


$$\tau = R_e C, \quad R_e = 15,000 \parallel 30,000 = 10 \text{ k}\Omega$$

$$\tau = (10 \times 10^3)(25 \times 10^{-9}) = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c = 7.5e^{-4000t} \text{ V}, \quad t \geq 0$$

$$v_c(0.2 \text{ ms}) = 7.5e^{-0.8} = 3.37 \text{ V}$$

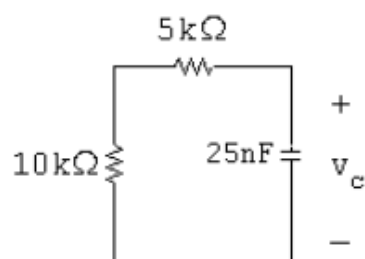
$0.2 \text{ ms} \leq t \leq 0.8 \text{ ms}$:



$$\tau = (15 \times 10^3)(2.5 \times 10^{-9}) = 375 \mu\text{s}, \quad \frac{1}{\tau} = 2666.67$$

$$v_c = 3.37e^{-2666.67(t-200 \times 10^{-6})} \text{ V}$$

$$0.8 \text{ ms} \leq t <:$$

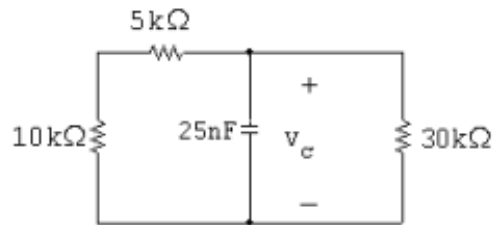

$$\tau = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c(0.8 \text{ ms}) = 3.37e^{-2666.67(800-200)10^{-6}} = 3.37e^{-1.6} = 0.68 \text{ V}$$

$$v_c = 0.68e^{-4000(t-0.8 \times 10^{-3})} \text{ V}$$


$$v_c(1 \text{ ms}) = 0.68e^{-4000(1-0.8)10^{-3}} = 0.68e^{-0.8} = 0.306 \text{ V}$$

$$v_o = (10/15)(0.306) = 0.204 \text{ V}$$

$$\frac{dv_c}{dt}(0^+) = \frac{1}{C} i_c(0^+)$$

$$\frac{di_L}{dt}(0^+) = \frac{1}{L} V_L(0^+)$$


in $t = 0^-$

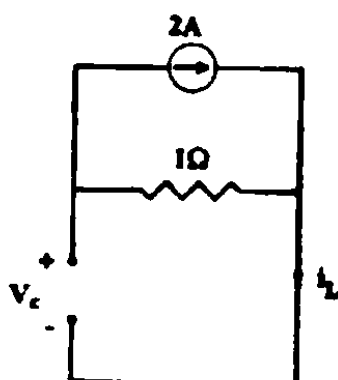

$$i_L(0) = 0$$

$$V_c(0) = -2$$


in $t = 0^+$

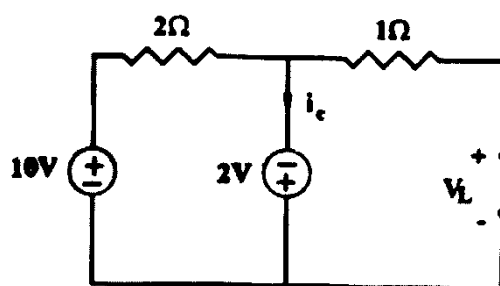

$$\begin{aligned} V_L(0^+) &= -2\text{V} \\ i_C(0^+) &= 6\text{A} \end{aligned} \Rightarrow \begin{cases} \frac{dV_C(0^+)}{dt} = 1 \times 6 = 6 \\ \frac{di_L(0^+)}{dt} = \frac{1}{1} \times -2 = -2 \end{cases}$$

For $t < 0$, $i(0) = 0$ and $v(0) = 0$.

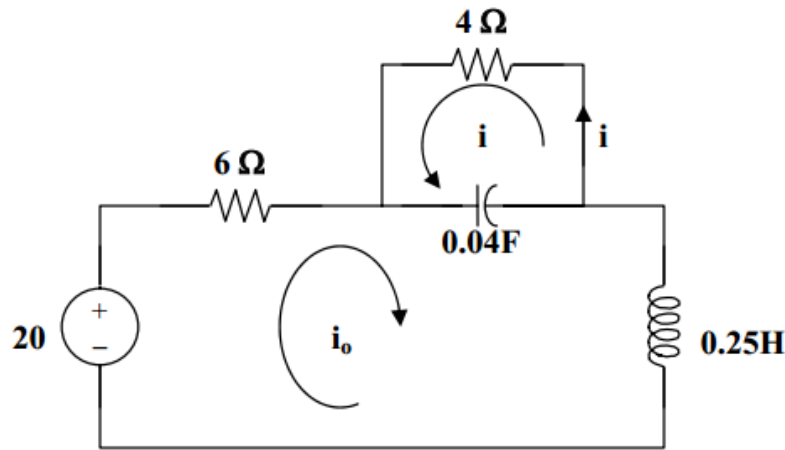For $t > 0$, the circuit is as shown below.



Applying KVL to the larger loop,

$$-20 + 6i_o + 0.25di_o/dt + 25 \int (i_o + i)dt = 0 \quad (1)$$

For the smaller loop, $4i + 25 \int (i + i_o)dt = 0$ or $\int (i + i_o)dt = -0.16i$ (2)

Taking the derivative, $4di/dt + 25(i + i_o) = 0$ or $i_o = -0.16di/dt - i$ (3)

and $di_o/dt = -0.16d^2i/dt^2 - di/dt$ (4)

From (1), (2), (3), and (4), $-20 - 0.96di/dt - 6i - 0.04d^2i/dt^2 - 0.25di/dt - 4i = 0$

Which becomes, $d^2i/dt^2 + 30.25di/dt + 250i = -500$

This leads to, $s^2 + 30.25s + 250 = 0$

$$\text{or } s_{1,2} = \frac{-30.25 \pm \sqrt{(30.25)^2 - 1000}}{2} = -15.125 \pm j4.608$$

This is clearly an underdamped response.

Thus, $i(t) = I_s + e^{-15.125t}(A_1\cos(4.608t) + A_2\sin(4.608t))A$.


At $t = 0$, $i_o(0) = 0$ and $i(0) = 0 = I_s + A_1$ or $A_1 = -I_s$. As t approaches infinity, $i_o(\infty) = 20/10 = 2A = -i(\infty)$ or $i(\infty) = -2A = I_s$ and $A_1 = 2$.

In addition, from (3), we get $di(0)/dt = -6.25i_o(0) - 6.25i(0) = 0$.

$di/dt = 0 - 15.125 e^{-15.125t}(A_1\cos(4.608t) + A_2\sin(4.608t)) + e^{-15.125t}(-A_1 4.608\sin(4.608t) + A_2 4.608\cos(4.608t))$. At $t=0$, $di(0)/dt = 0 = -15.125A_1 + 4.608A_2 = -30.25 + 4.608A_2$ or $A_2 = 30.25/4.608 = 6.565$.

This leads to,
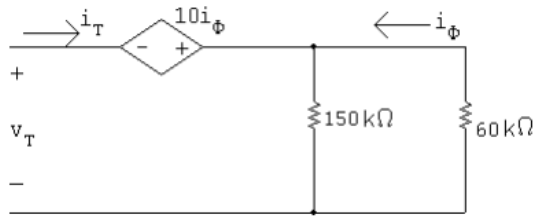
$$i(t) = \underline{(-2 + e^{-15.125t}(2\cos(4.608t) + 6.565\sin(4.608t))) A}$$



$$v_T = -10i_\phi + i_T \left(\frac{(150)(60)}{210} \right) = -10 \frac{-i_T(150)}{210} + i_T \frac{9000}{210}$$

$$\frac{v_T}{i_T} = \frac{1500 + 9000}{210} = 50 \, \Omega$$

$$V_o = \frac{4000}{10,000}(50) = 20 \, \text{V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{20}{50} = -0.4 \, \text{A}$$

$$\frac{i_C(0)}{C} = \frac{-0.4}{8 \times 10^{-6}} = -50,000$$

$$\omega_o = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(51.2 \times 10^{-3})(8 \times 10^{-6})}} = 1562.5 \, \text{rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(50)(8 \times 10^{-6})} = 1250 \, \text{rad/s}$$

$$\alpha^2 < \omega_0^2 \quad \text{so the response is underdamped}$$

$$\omega_d = \sqrt{1562.5^2 - 1250^2} = 937.5$$


$$v_o = B_1 e^{-1250t} \cos 937.5t + B_2 e^{-1250t} \sin 937.5t$$

$$v_o(0) = B_1 20 \, \text{V}$$

$$\frac{dv_o}{dt}(0) = -\alpha B_1 + \omega_d B_2 = \frac{i_C(0)}{C}$$

$$\therefore \quad -1250(20) + 937.5 B_2 = -50,000 \quad \text{so} \quad B_2 = -26.67$$
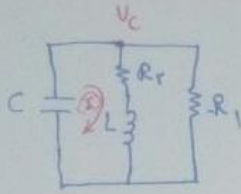
$$v_o = 20e^{-1250t} \cos 937.5t - 26.67e^{-1250t} \sin 937.5t \, \text{V}, \quad t \geq 0$$



$$(KCL) \Rightarrow i_c + i_L + \frac{V_c}{-R_i} = 0$$

$$C \frac{dV_c}{dt} + i_L - \frac{V_c}{R_i} = 0 \quad (1)$$

$$(KVL)_{\text{I}} \Rightarrow V_c = R_r i_L + L \frac{di_L}{dt} \quad (2)$$

$$\text{I, 2} \Rightarrow R_r C \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} + i_L - \frac{R_r}{R_i} i_L - \frac{L}{R_i} \frac{di_L}{dt} = 0$$

$$LC \frac{d^2 i_L}{dt^2} + \left(R_r C - \frac{L}{R_i} \right) \frac{di_L}{dt} + \left(1 - \frac{R_r}{R_i} \right) i_L = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{LC} \left(R_r C - \frac{L}{R_i} \right) \frac{di_L}{dt} + \frac{1}{LC} \left(1 - \frac{R_r}{R_i} \right) i_L = 0$$

$$\left. \begin{array}{l} \gamma_d = 0 \\ \omega_d > 0 \end{array} \right\}$$

شماره های زوج

$$\gamma_d = \frac{1}{LC} \left(R_r C - \frac{L}{R_i} \right) = 0$$

$$R_i = \frac{L}{R_r C}$$

$$\omega_d = \frac{1}{LC} \left(1 - \frac{R_r}{R_i} \right) > 0$$

$$R_i > R_r$$